

Electricity

HW# 8

Name: _____

Class: 8 ____

Date: _____

For the following circuit find

- A) Equivalent resistor.
- B) the current drawn from the battery.
- C) Current flowing through R_1 , R_2 , and R_3 .
- D) Power consumed by each resistor.

