

PRACTICE A

Resistors in Series

4. A series combination of two resistors, $7.25\ \Omega$ and $4.03\ \Omega$, is connected to a $9.00\ \text{V}$ battery.
- Calculate the equivalent resistance of the circuit and the current.
 - What is the potential difference across each resistor?