

Circuits

HW# 9

Name: \_\_\_\_\_

Class: 8 \_\_\_\_

Date: \_\_\_\_\_

Given the circuit

- Draw the current flow on the circuit. Label each current
- Find the equivalent resistance,  $R_{eq}$ , of the circuit

