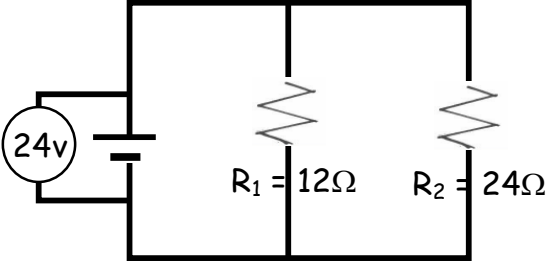
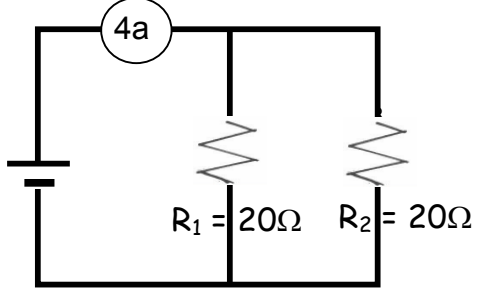
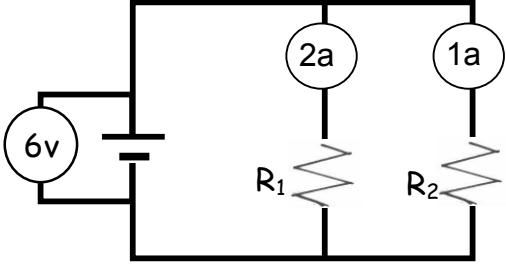
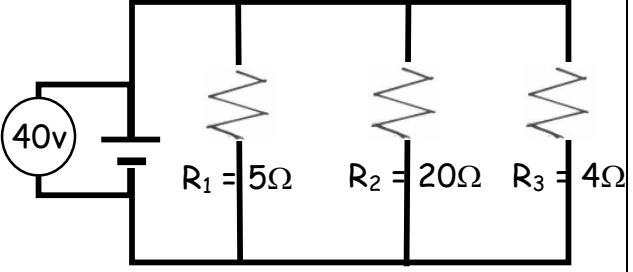
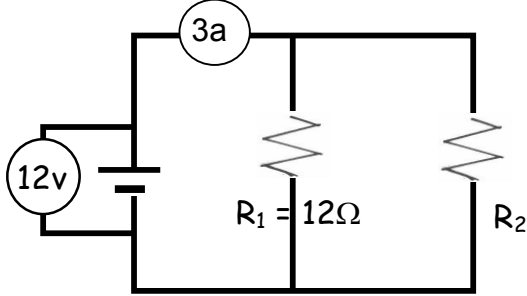
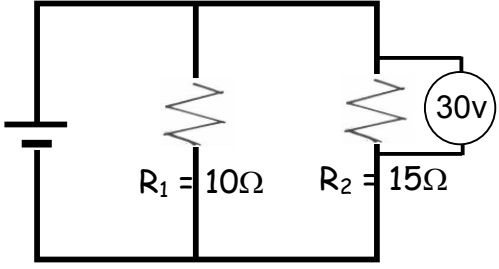


Remember that in a parallel circuit:

- the **current** in the branches of the circuit (is the same, adds up).
- the **voltage** drops across each branch (is the same, adds up to) the total voltage.
- to calculate total **resistance**, (add, use reciprocals).

 <p style="margin-top: 10px;"> $R_{eq} = \underline{\hspace{2cm}}$ $I_T = \underline{\hspace{2cm}}$ $V_1 = \underline{\hspace{2cm}}$ $V_2 = \underline{\hspace{2cm}}$ $I_1 = \underline{\hspace{2cm}}$ $I_2 = \underline{\hspace{2cm}}$ </p>	 <p style="margin-top: 10px;"> $R_{eq} = \underline{\hspace{2cm}}$ $I_T = \underline{\hspace{2cm}}$ $V_T = \underline{\hspace{2cm}}$ $V_1 = \underline{\hspace{2cm}}$ $I_1 = \underline{\hspace{2cm}}$ $I_2 = \underline{\hspace{2cm}}$ </p>
 <p style="margin-top: 10px;"> $V_1 = \underline{\hspace{2cm}}$ $V_2 = \underline{\hspace{2cm}}$ $R_1 = \underline{\hspace{2cm}}$ $R_2 = \underline{\hspace{2cm}}$ $R_{eq} = \underline{\hspace{2cm}}$ $I_1 = \underline{\hspace{2cm}}$ $I_2 = \underline{\hspace{2cm}}$ $I_T = \underline{\hspace{2cm}}$ </p>	 <p style="margin-top: 10px;"> $R_{eq} = \underline{\hspace{2cm}}$ $I_T = \underline{\hspace{2cm}}$ $V_1 = \underline{\hspace{2cm}}$ $V_2 = \underline{\hspace{2cm}}$ $V_3 = \underline{\hspace{2cm}}$ $I_1 = \underline{\hspace{2cm}}$ $I_2 = \underline{\hspace{2cm}}$ $I_3 = \underline{\hspace{2cm}}$ </p>
 <p style="margin-top: 10px;"> $V_1 = \underline{\hspace{2cm}}$ $V_2 = \underline{\hspace{2cm}}$ $I_T = \underline{\hspace{2cm}}$ $I_1 = \underline{\hspace{2cm}}$ $I_2 = \underline{\hspace{2cm}}$ $R_2 = \underline{\hspace{2cm}}$ $R_{eq} = \underline{\hspace{2cm}}$ </p>	 <p style="margin-top: 10px;"> $V_1 = \underline{\hspace{2cm}}$ $V_T = \underline{\hspace{2cm}}$ $I_1 = \underline{\hspace{2cm}}$ $I_2 = \underline{\hspace{2cm}}$ $R_{eq} = \underline{\hspace{2cm}}$ $I_T = \underline{\hspace{2cm}}$ </p>